

AC 88

1.5.1 Binary adders with parity control

- use parity control for protecting adders against errors
- attach 1 parity bit to operands.

$$X, Y, c_0 \rightarrow Z, Z = X + Y + c_0$$

inputs:
$$\begin{cases} x_p = x_{n-1} \oplus x_{n-2} \oplus x_{n-3} \oplus \dots \oplus x_1 \oplus x_0 \\ y_p = y_{n-1} \oplus y_{n-2} \oplus \dots \oplus y_1 \oplus y_0 \end{cases}$$

$$z_p = z_{n-1} \oplus z_{n-2} \oplus \dots \oplus z_1 \oplus z_0 \quad (1)$$

$$z_i = x_i \oplus y_i \oplus c_i$$

← generate →

Notation $c_p = c_{n-1} \oplus c_{n-2} \oplus \dots \oplus c_1 \oplus c_0$


← propagate →

$$z_p = x_{n-1} \oplus y_{n-1} \oplus c_{n-1} \oplus x_{n-2} \oplus y_{n-2} \oplus c_{n-2} \oplus \dots \oplus x_0 \oplus y_0 \oplus c_0$$

$$z_p = x_p \oplus y_p \oplus c_p \quad (2)$$

- faster than (1)
- anticipates value of z_p (1)

Verify $z_p(1) == z_p(2)$

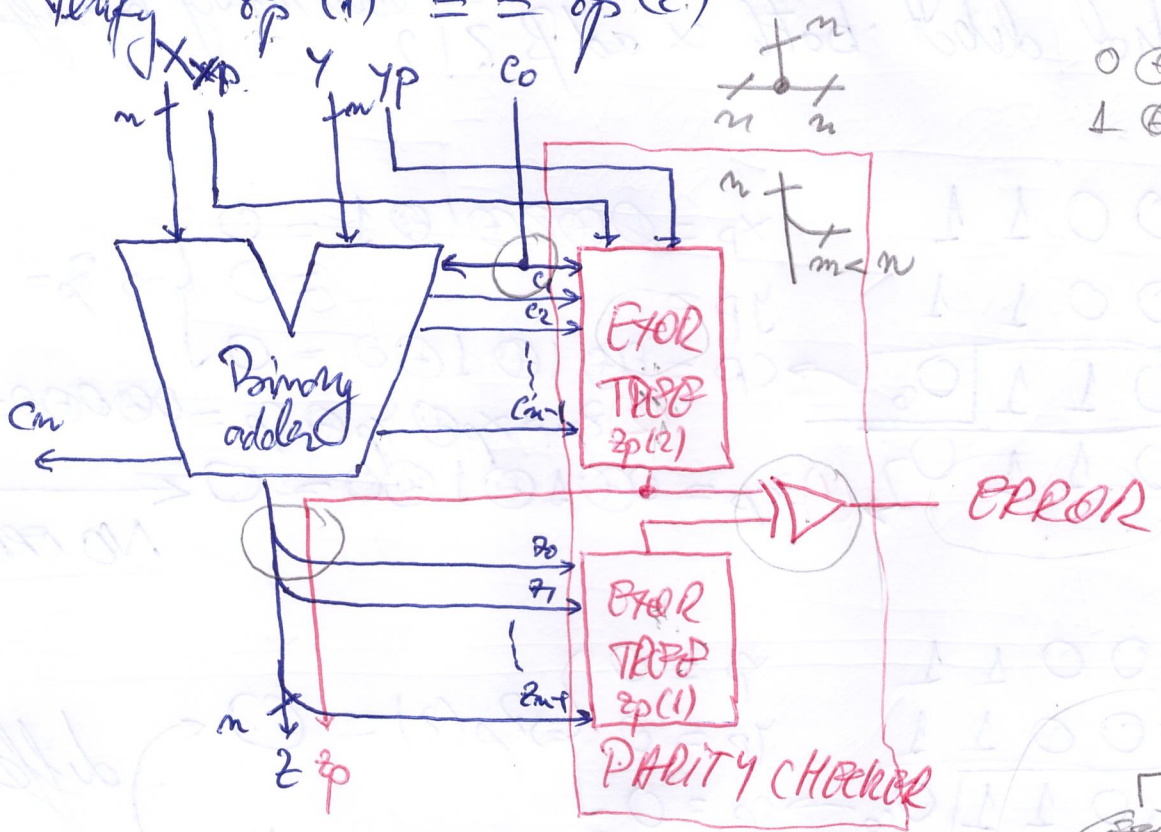


$$\begin{aligned} 0 \oplus 0 &\rightarrow 0 \\ 1 \oplus 1 &\rightarrow 0 \end{aligned}$$

Parity checker = EXOR tree



ERRORS that can affect a binary adder:

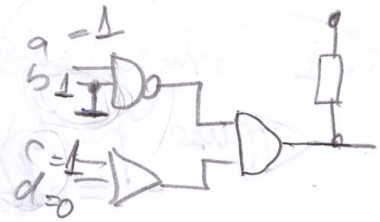
- errors \rightarrow single: \rightarrow higher probability
- multiple: \rightarrow harder to detect



logic manifestation

Single Stuck at Fault (SSaF)

RCA - 4 bits

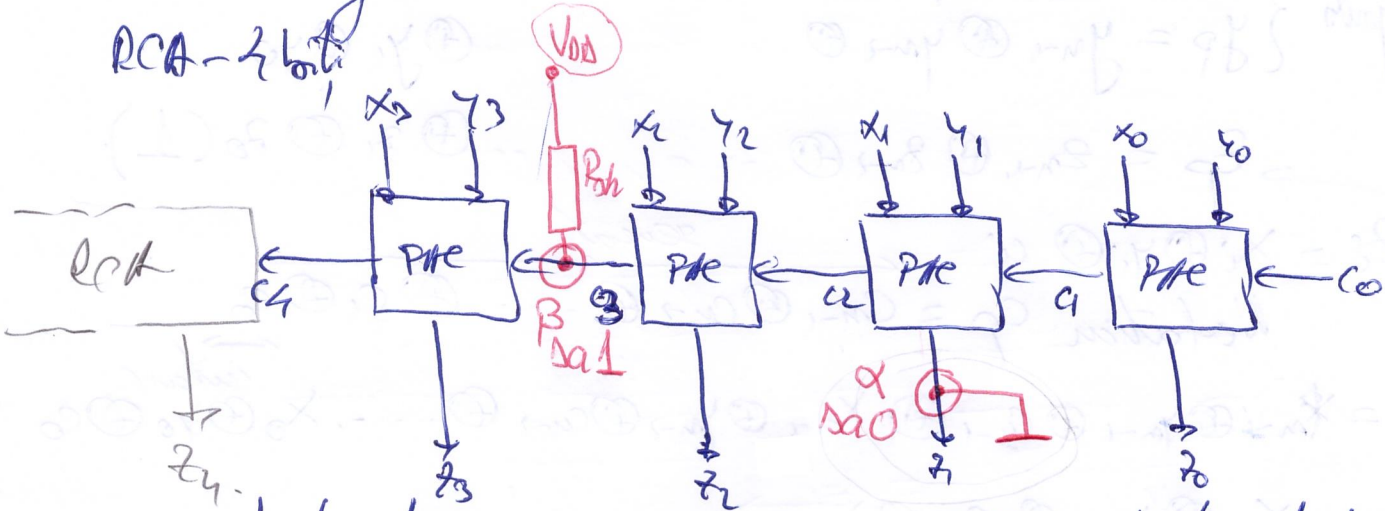

α : stuck-at 0

only z_1 is affected.
 \Rightarrow odd no of bits affected.

β : stuck-at 1

c_3, z_3 = affected.
 - possibly c_4, z_4
 \Rightarrow even no of bits affected

Can parity control detect both α and β ? !?

fault-free

$$X = 0011$$

$$x_p = 0 \oplus 0 \oplus 1 \oplus 1 = 0$$

$$Y = 0011$$

$$y_p = 0 \oplus 0 \oplus 1 \oplus 1 = 0$$

$$c = c_4 \quad 0 \quad 1 \quad 1 \quad 0_{c_0}$$

$$c_p = 0 \oplus 1 \oplus 1 \oplus 0 = 0$$

$$z = 0 \quad 1 \quad 1 \quad 0$$

$$(2) z_p = x_p \oplus y_p \oplus c_p = 0 \oplus 0 \oplus 0 = 0$$

$$(1) z_p = 0 \oplus 1 \oplus 1 \oplus 0 = 0$$

NO ERROR

$\alpha: z_1 \text{ Sa0}$

$$X = 0011$$

$$x_p = 0$$

$$Y = 0011$$

$$y_p = 0$$

$$c = c_4 \quad 0 \quad 1 \quad 1 \quad 0_{c_0}$$

$$c_p = 0$$

$$z = 0 \quad 1 \quad 0 \quad 0$$

$$z_p(2) = 0$$



$$z_p(1) = 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

! ERROR


NO ERROR?!?

Solution: \rightarrow carry chain duplication
 \rightarrow Carry Dependent Sum Adder

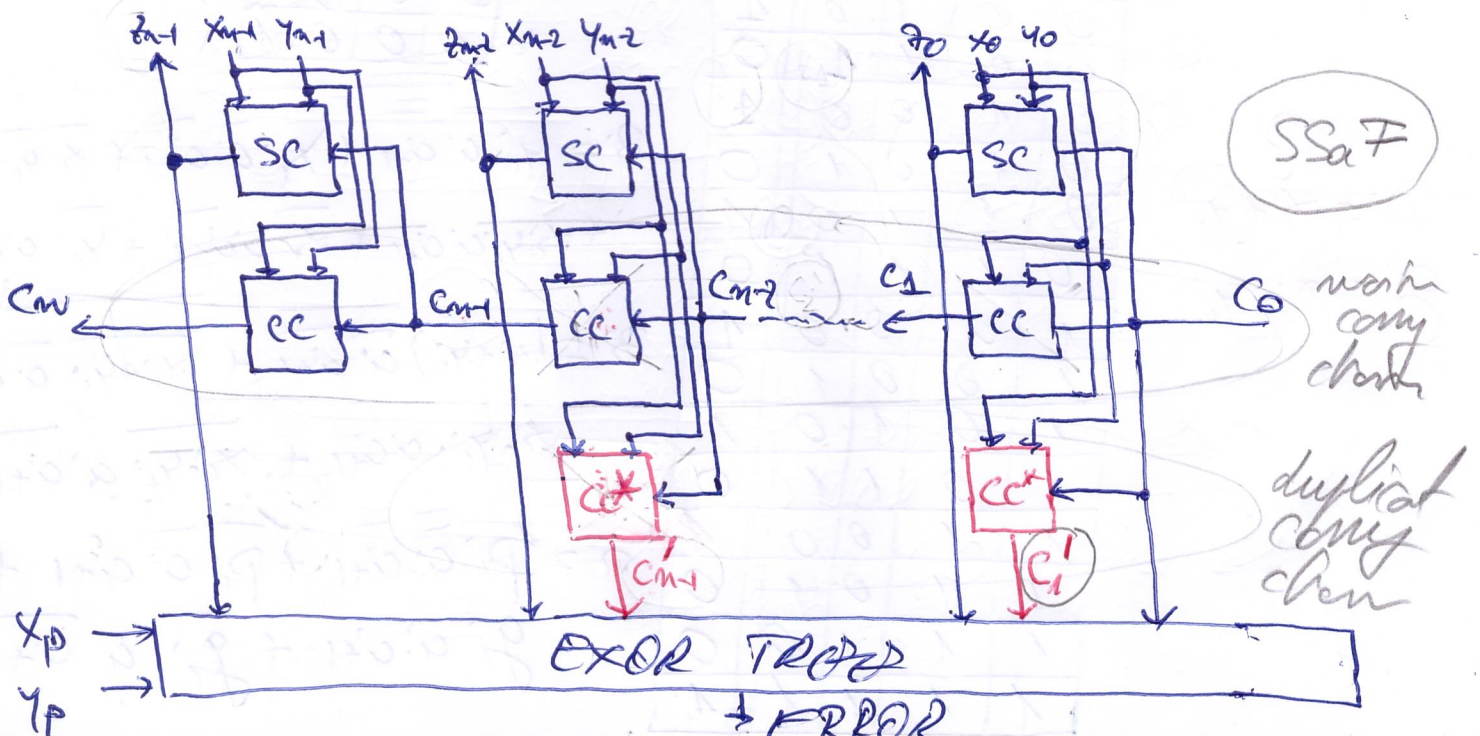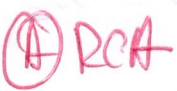- adds on additional copy chain
- used for calculating $g_p(?)$
- split PHE in 2 cells




③ CLA

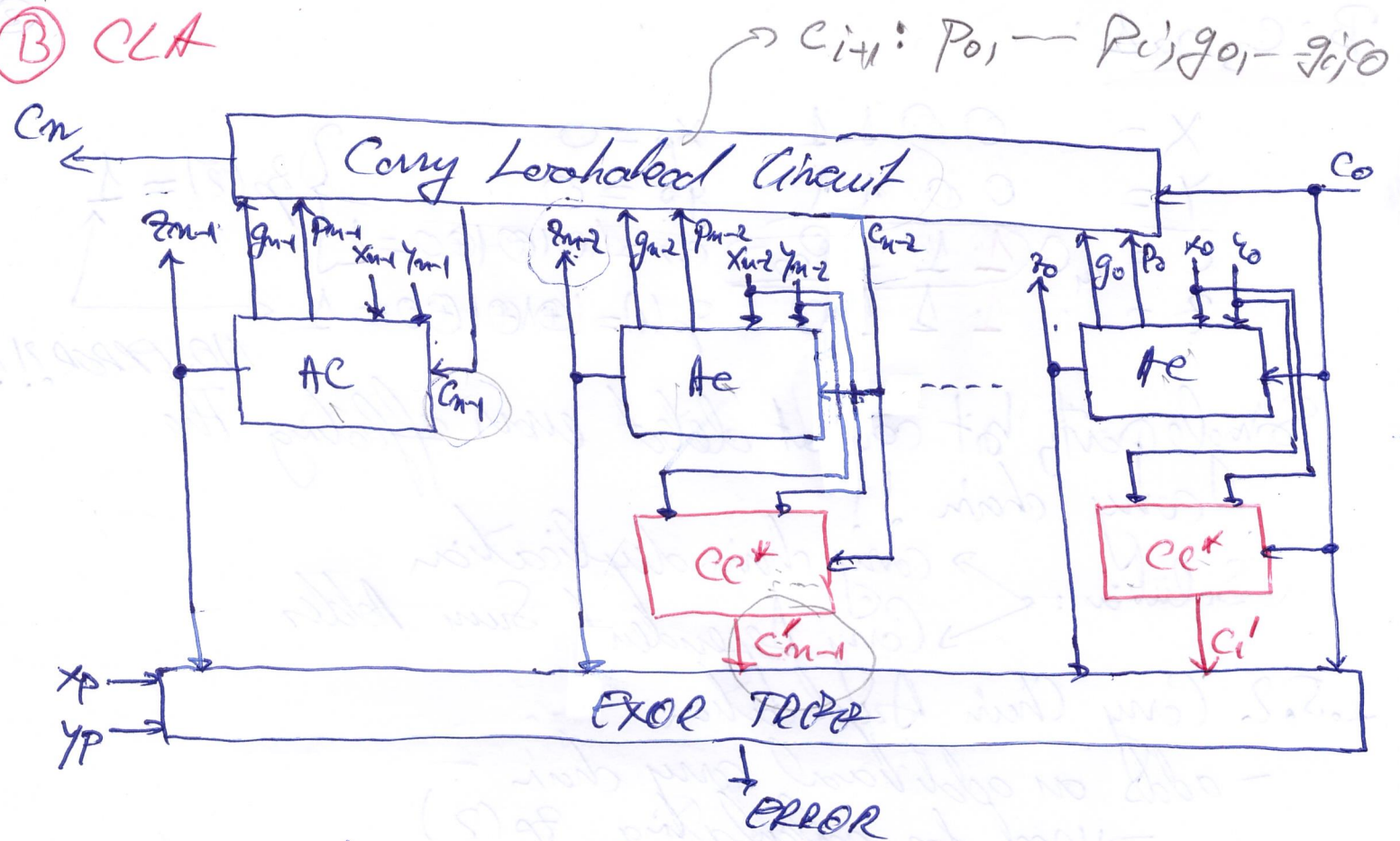

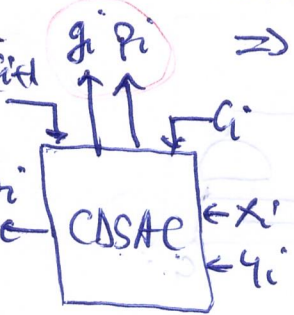1.5.3. Carry Dependent Sum Adder. (CDSA)

- address reliability from design phase
- if C_{i+1} is incorrect \rightarrow force Z_i take incorrect





$P_i = x_i + y_i$
 $G_i = x_i \cdot y_i$

Inputs				Output
x_i	y_i	G_i	P_i	Z_i
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

x_i	y_i	G_i	P_i	Z_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$\overline{a} \cdot \overline{b} = \overline{a+b}$
 $\overline{a} + \overline{b} = \overline{a \cdot b}$

$Z_i = y_i \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{x_i} \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{x_i} \cdot y_i \cdot \overline{a_i} \cdot \overline{a_{i+1}}$
 $+ \overline{x_i} \cdot y_i \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{x_i} \cdot \overline{a_i} \cdot \overline{a_{i+1}} + y_i \cdot \overline{a_i} \cdot \overline{a_{i+1}}$
 $Z_i = (x_i + y_i) \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{x_i + y_i} \cdot \overline{a_i} \cdot \overline{a_{i+1}} +$
 $x_i \cdot y_i \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{x_i} \cdot \overline{y_i} \cdot \overline{a_i} \cdot \overline{a_{i+1}}$
 $Z_i = P_i \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{P_i} \cdot \overline{a_i} \cdot \overline{a_{i+1}} +$
 $G_i \cdot \overline{a_i} \cdot \overline{a_{i+1}} + \overline{G_i} \cdot \overline{a_i} \cdot \overline{a_{i+1}}$

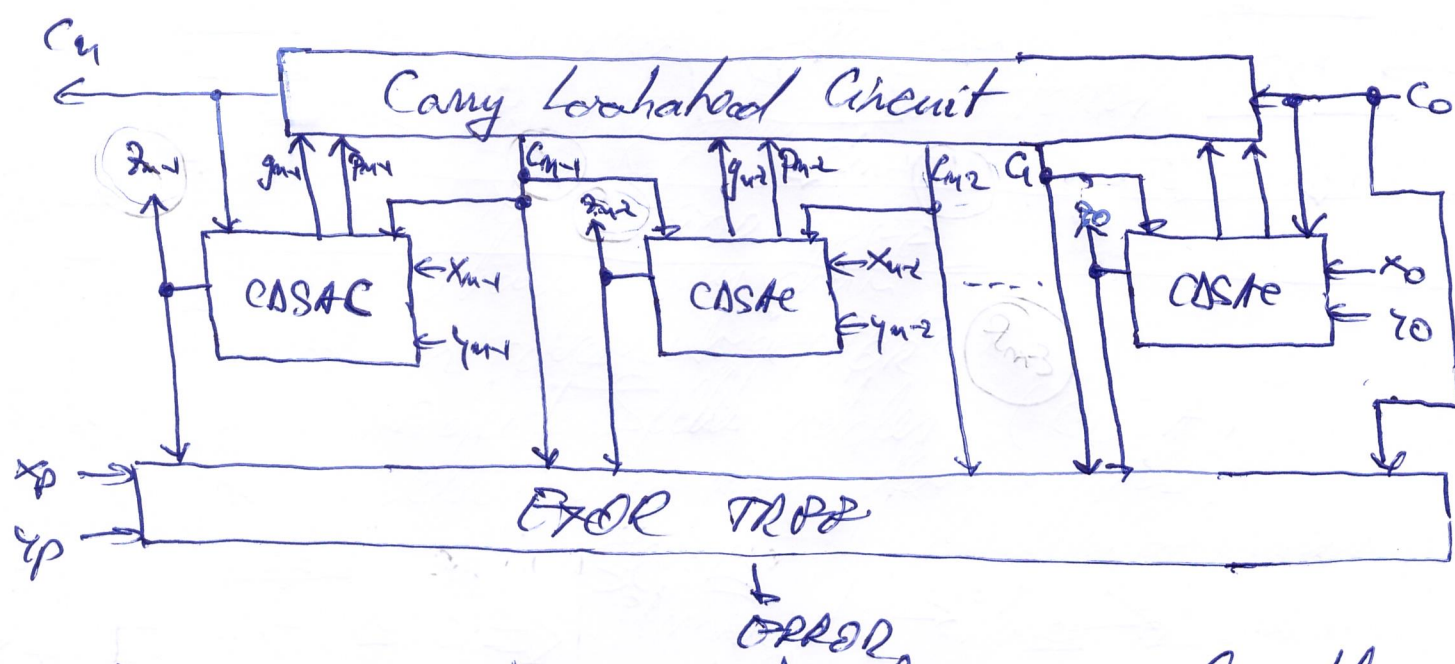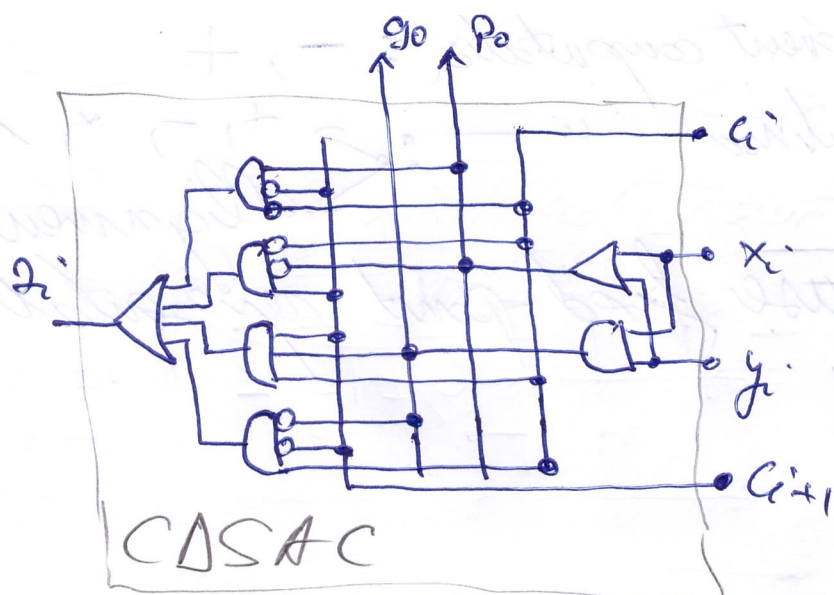

Chapter 2 Functional Analysis and Synthesis of Floating Point Arithmetic Units

2.1. F.p. arithmetic operations and architecture
IEEE 754

packed (normalised): storage / transmission
 unpacked: during computations
 let $X = X_n \times 2^{x_e}$ $Y = Y_n \times 2^{y_e}$ \rightarrow alignment
 $X + Y = (X_n \oplus Y_n \times 2^{y_e - x_e}) \times 2^{x_e}$, if $x_e \geq y_e$
 $X - Y = (X_n \ominus Y_n \times 2^{y_e - x_e}) \times 2^{x_e}$, if $x_e \geq y_e$
 $X * Y = X_n \otimes Y_n \times 2^{x_e + y_e}$
 $\frac{X}{Y} = \frac{X_n}{Y_n} \times 2^{x_e - y_e}$

