

Ae CB

### 3.3. Excitation and output equations


- derived from flowchart directly

Consider using D type flip-flop

State variables:  $B_0, B_1, \dots, B_7$

State encoding:

State	$D_7$	$B_0$	$B_1$	$B_2$	$B_3$	$B_4$	$B_5$	$B_6$
$S_0$	0	0	0	0	0	0	0	1
$S_1$	0	0	0	0	0	0	1	0
$S_2$	0	0	0	0	0	1	0	0
$S_3$	0	0	0	0	1	0	0	0
$S_4$	0	0	0	1	0	0	0	0
$S_5$	0	0	1	0	0	0	0	0
$S_6$	0	1	0	0	0	0	0	0
$S_7$	1	0	0	0	0	0	0	0

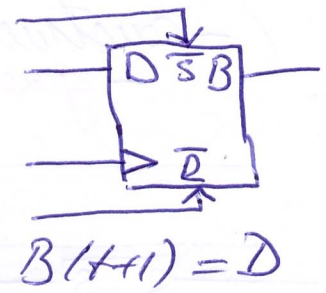

Excitation equation

$$D_0 = B_0 \cdot \text{BEGIN} \text{ or } B_7$$

$$D_1 = B_0 \cdot \text{BEGIN}$$

$$D_2 = B_1$$

$$D_3 = B_2 \cdot \text{QTO} \text{ or } B_4 \cdot \text{COUNT} \cdot \text{QTO}$$

$$D_4 = B_2 \cdot \text{QTO} \text{ or } B_3 \text{ or } B_4 \cdot \text{COUNT} \cdot \text{QTO}$$

$$D_5 = B_4 \cdot \text{COUNT}$$

$$D_6 = B_5$$

$$D_7 = B_6$$

Output equations

$$\text{END} = B_0$$

$$C_0 = B_1$$

$$C_1 = B_2$$


$$C_2 = B_3$$

$$C_3 = B_4$$

$$C_4 = B_5$$

$$C_5 = B_6$$


$$C_6 = B_7$$

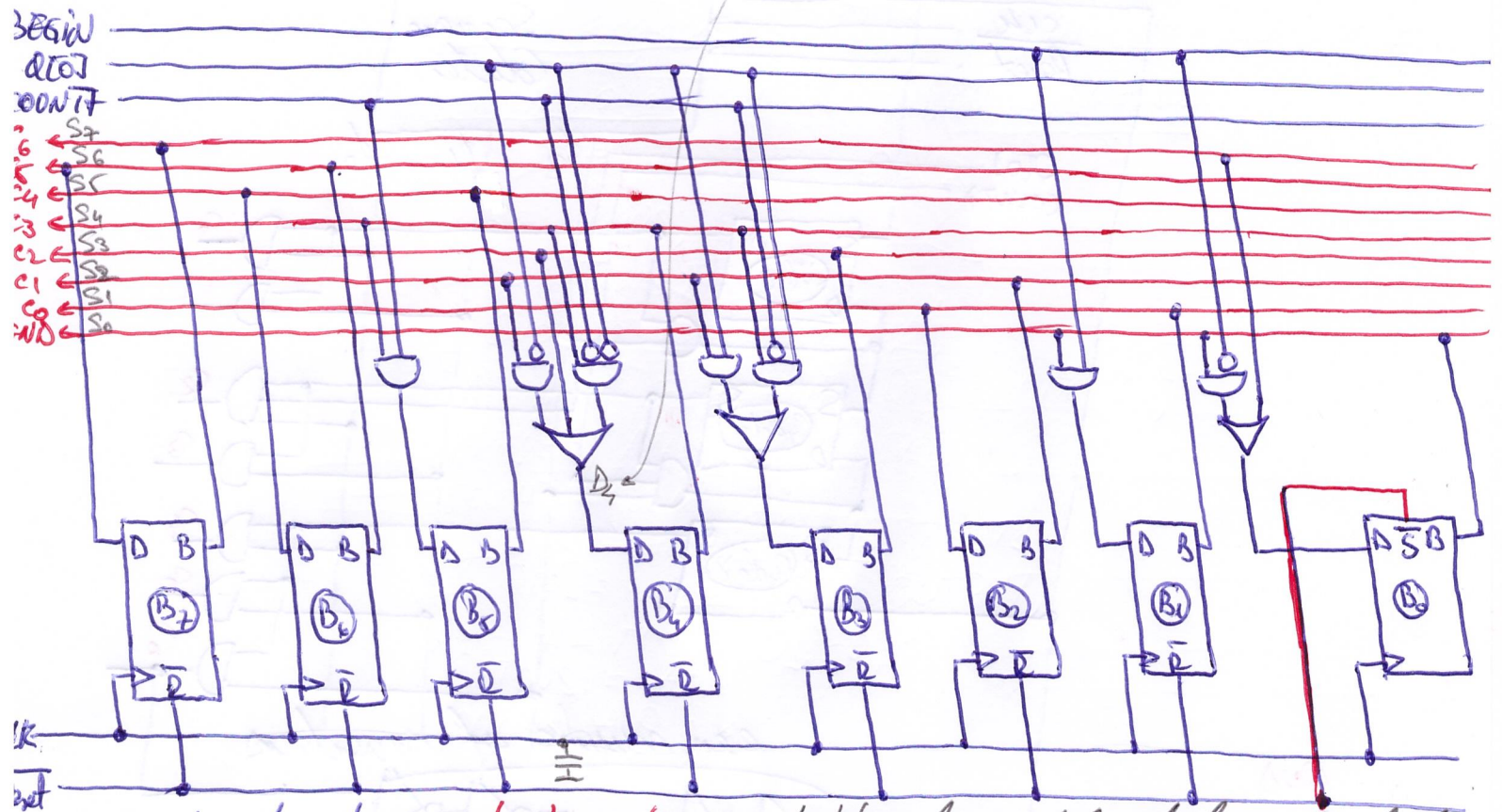

- disconnection: clock when clock's edge is delayed for some time.




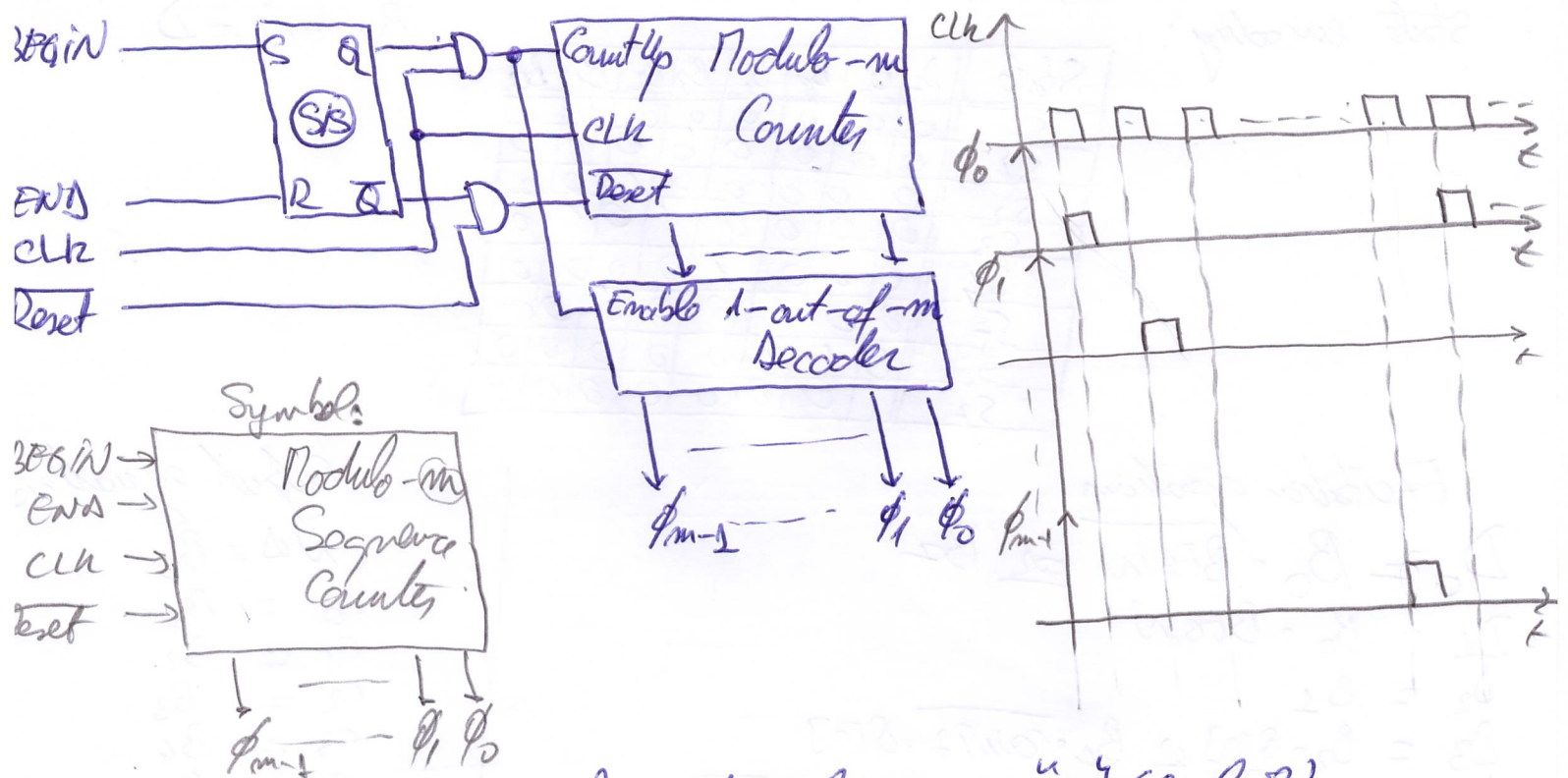- ③ Sequence Counter
- constructed around a Sequence Counter
  - generates non-overlapping, synchronous pulses



Determine value of  $m$ : longest cycle:  $m = 3^4$  (Cycle 8)

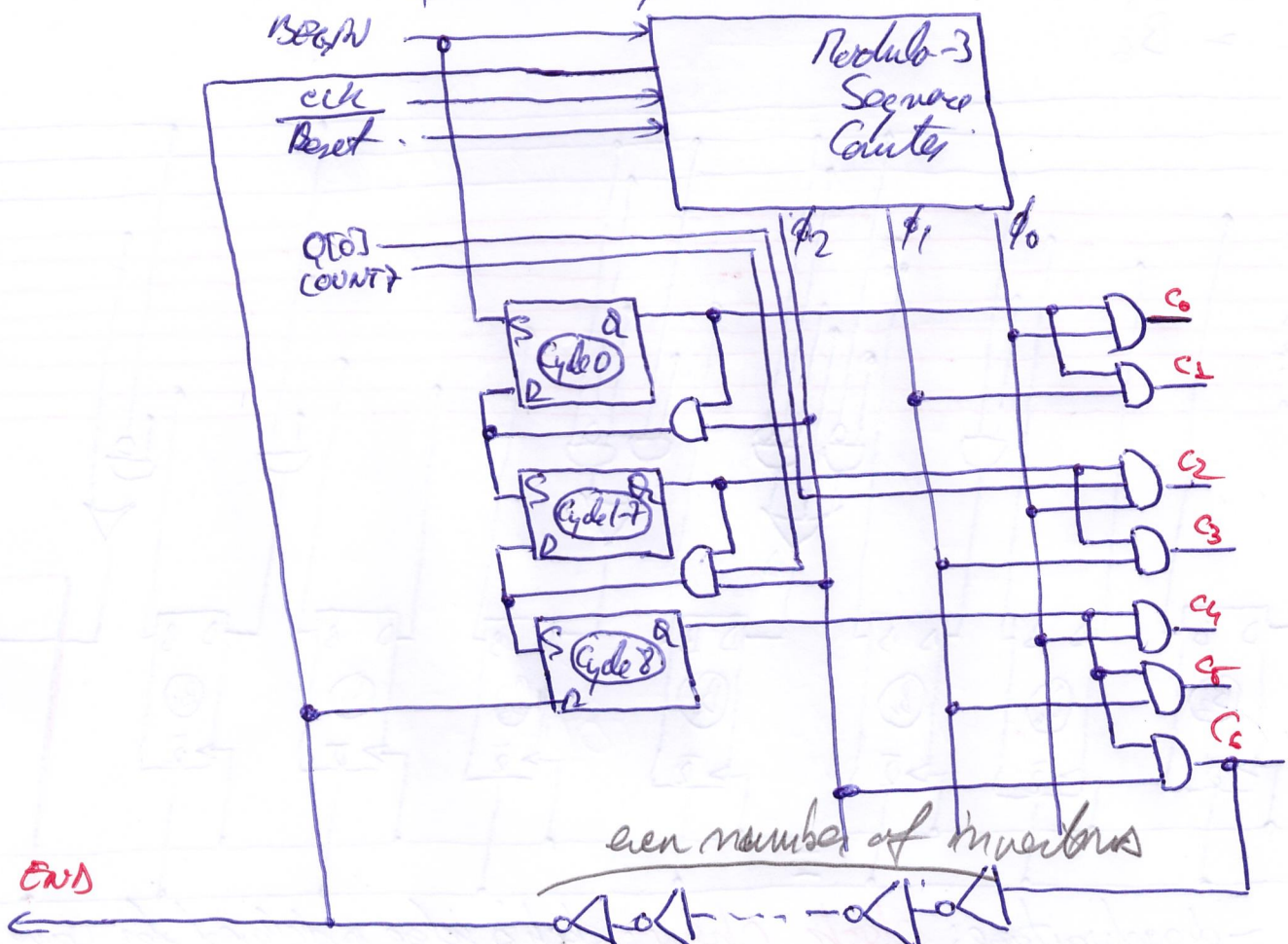Provide one SR latch for each cycle; active in the respective cycle.





### 3.4. Two's Complement Multiplication Based on Robert's Procedure. ②

Robert's interpretation: the value of a number in C2 is equal with the value of the positive number obtained by clearing its sign bit from which is subtracted the weight associated with the sign bit.

Example:  $X = \underset{2^3}{1}011_{C2} \rightarrow X = \overset{\text{positive SN}}{0011}_{C2} - 1 \cdot 2^3 = 3 - 8 = -5$

$1011_{C2} \rightarrow \overset{\text{complement}}{1010}_{C1} \rightarrow \underline{1101}_{SN} = -5$

$X_{\text{integer}}: X = \underset{2^3}{0}101_{C2} \rightarrow X = \underset{\text{positive SN}}{0101}_{C2} - 0 \cdot 2^3 = 5 - 0 = 5$

Multiplication of C2 can be obtained:

- 1) convert C2 → SN for  $X, Y$  (2x)
- 2) multiply  $X * Y = P$  in SN. (1x), double weight
- 3) convert SN → C2 for  $P$

Let  $X_{C2} = \overset{\text{fractional}}{x_{n-1}} x_{n-2} \dots x_1 x_0$

for  $X_{\text{integer}}$   $X = \underbrace{-x_{n-1} \cdot 2^{n-1}}_{\text{CORRECTION}} + \underbrace{0 x_{n-2} \dots x_1 x_0}_{\text{positive in C2, SN}}$

for  $X_{\text{fractional}}$   $X = \underbrace{-x_{n-1} \cdot 2^0}_{\text{CORRECTION}} + \underbrace{0 x_{n-2} \dots x_1 x_0}_{\text{positive in C2, SN}}$

A positive in C2  $\equiv$  A positive in SN

A negative in C2  $\equiv$  A positive in SN + CORRECTION

$P = X_{C2} * Y = (0 x_{n-2} \dots x_1 x_0 - \underbrace{x_{n-1} \cdot 2^0}_{\text{CORRECTION}}) * Y$

for  $X, Y$  - fractionals)  $\uparrow$

$= \underbrace{X_{SN}^*}_{\text{positive}} * Y - x_{n-1} * Y \cdot 2^0$

$\rightarrow$  multiplication in SN.

Multiplicand  $Y$  can also be a C2 negative:

$\Rightarrow$  all partial products have sign

- they have the sign of  $Y$

$\rightarrow$  accumulator  $A$  will now store the sign.



# multiplexer 3

declare registers  $A[7:0], Q[7:0], N[7:0], COUNT[0], F;$

declare bus  $INBUS[7:0], OUTBUS[7:0];$

BEGIN:  
INPUT:

$A := 0, COUNT := 0, F := 0;$   
 $N := INBUS;$

TEST1:

$Q := INBUS;$   
if  $Q[0] = 0$  then go to RShift;

ADD:

$A := A + M, F := F \text{ or } (Q[0] \text{ and } N[7]);$

RShift:

$A[7] := F, A[6:0], Q := A.Q[7:1];$

INCREMENT:

$COUNT := COUNT + 1;$

TEST2:

if  $COUNT \neq 1$  then go to TEST1;

TEST3:

if  $Q[0] = 0$  then go to OUTPUT;


CORRECTION:

$A := A - M, Q[0] := 0;$

OUTPUT:

$OUTBUS := A;$   
 $OUTBUS := Q;$

END

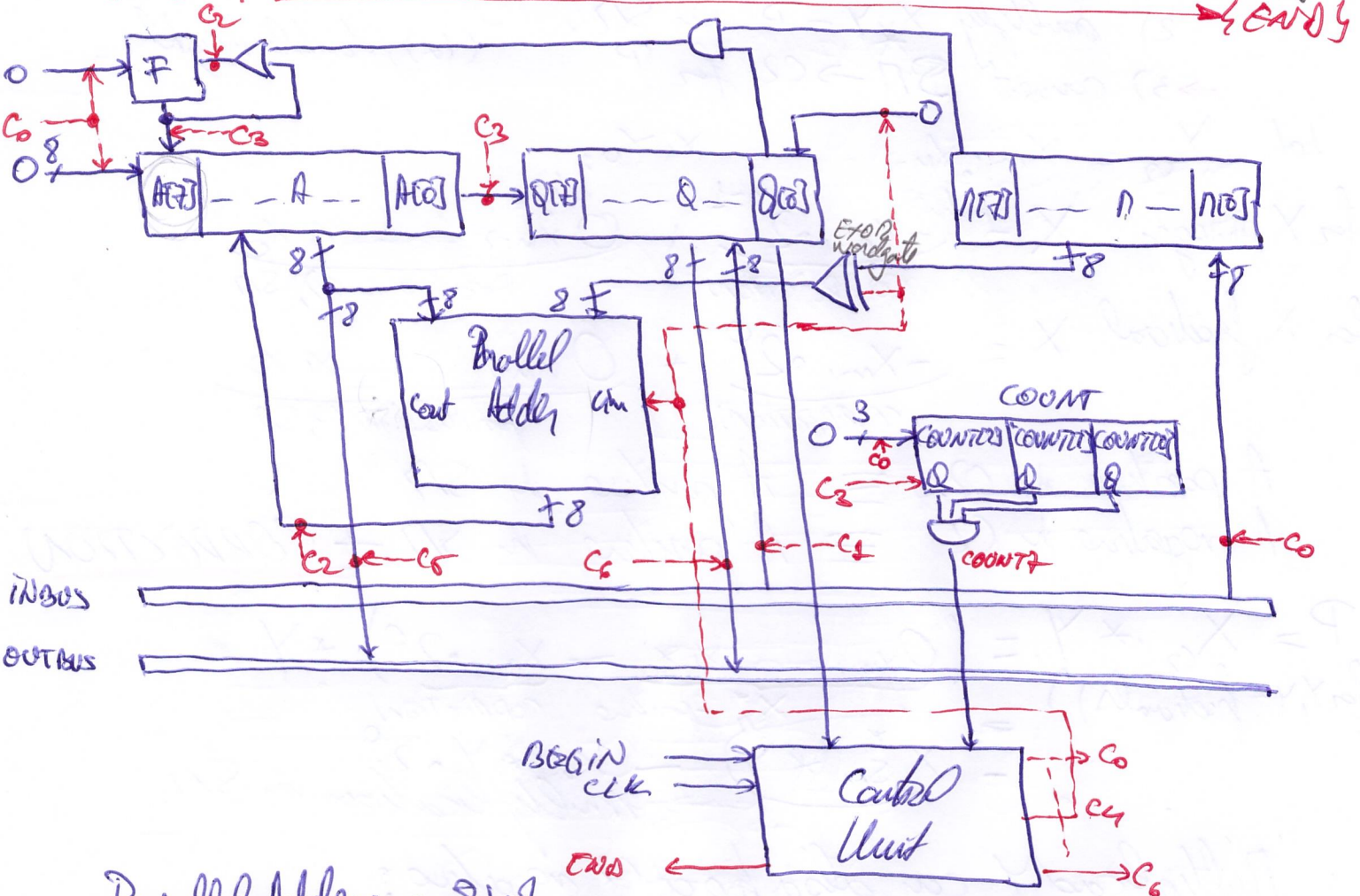

Parallel Adder: an 8 bits

-Carry: ignored!


$$V = C_n \oplus C_{n-1}$$

Q: Can overflow occur? How is it treated?!

A: At RShift, A is restoring its sign from flag F.

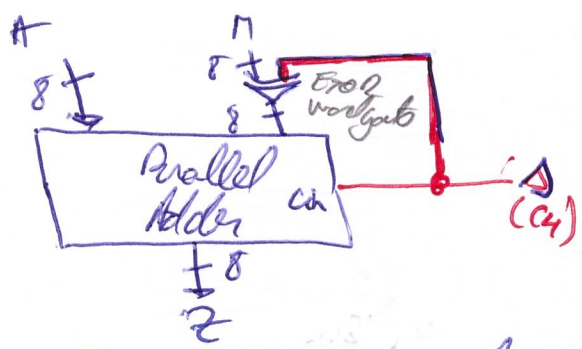In flag F: store the correct sign of partial products.  
- is part of a adder/subtractor.





$0: Z = A + B$   
 $1: Z = A - B$

Flag F: stores the sign of partial products.

Q: why not use MTF (sign of Y)?

A: as long as  $P_i = 0, i \geq 0$  sign of those  $P_i$  must be 0, not MTF

after  $P_i$  becomes  $\neq 0$ , F is set to MTF

Q: which partial product,  $P_i$ , is  $\neq 0$ ? !?

- the one for which  $x_i$  (stored in Q[10])

$c_{10} x_i = 1$

$P_i = P_i + X \cdot Y$   
 $P_{i+1} = P_i \cdot 2^{-1}$


Sign of result is not set.

- operating in C2 generates correct result sign.

Depending on the signs of the 2 operands, algorithm performs the following operations

Example:  $X = -0.75 = 1.110_{sn} = 1.010_{c2}$   
 $Y = -0.875 = 1.111_{sn} = 1.001_{c2}$

$x_7$	$y_7$	CORRECTION STOP	ARITHMETIC RSHIFT
0	0	NO	NO
0	1	NO	YES
1	0	YES	NO
1	1	YES	YES

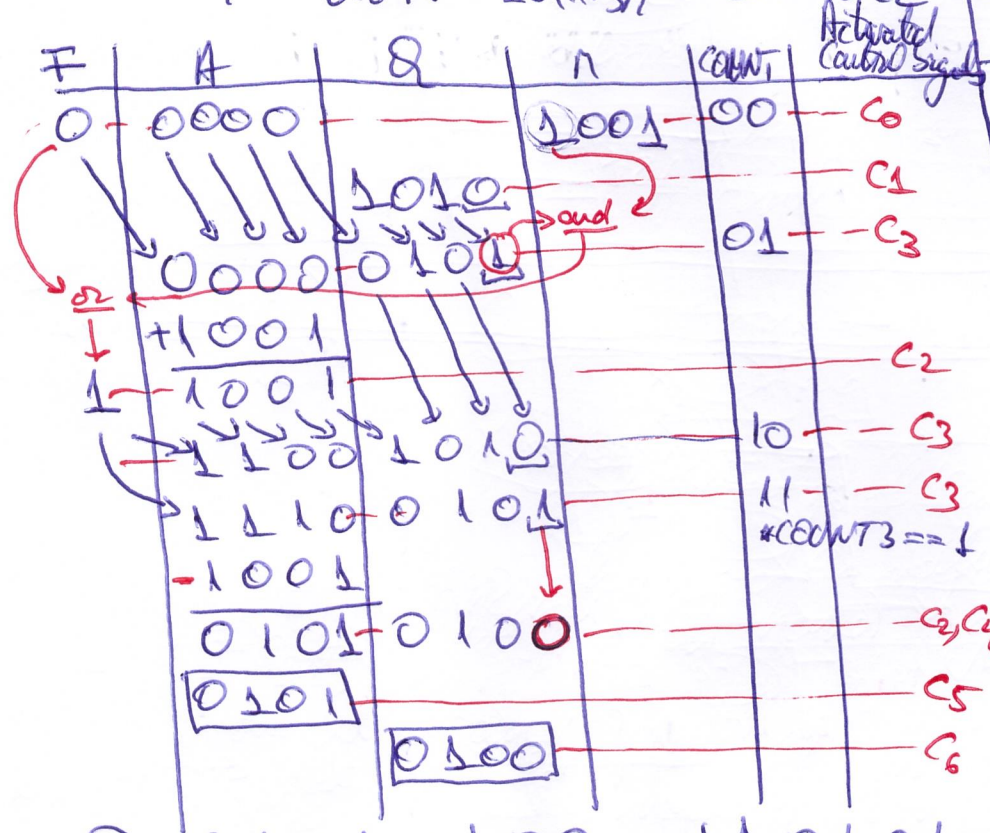

$P = 0.1010100 = +10101 \times 2^{-5} = +21 \cdot 2^{-5}$   
 $X = -3 \times 2^{-2} \quad Y = -7 \times 2^{-3} \quad P = (-3) \times 2^{-2} \times (-7) \times 2^{-3} = +21 \times 2^{-5}$