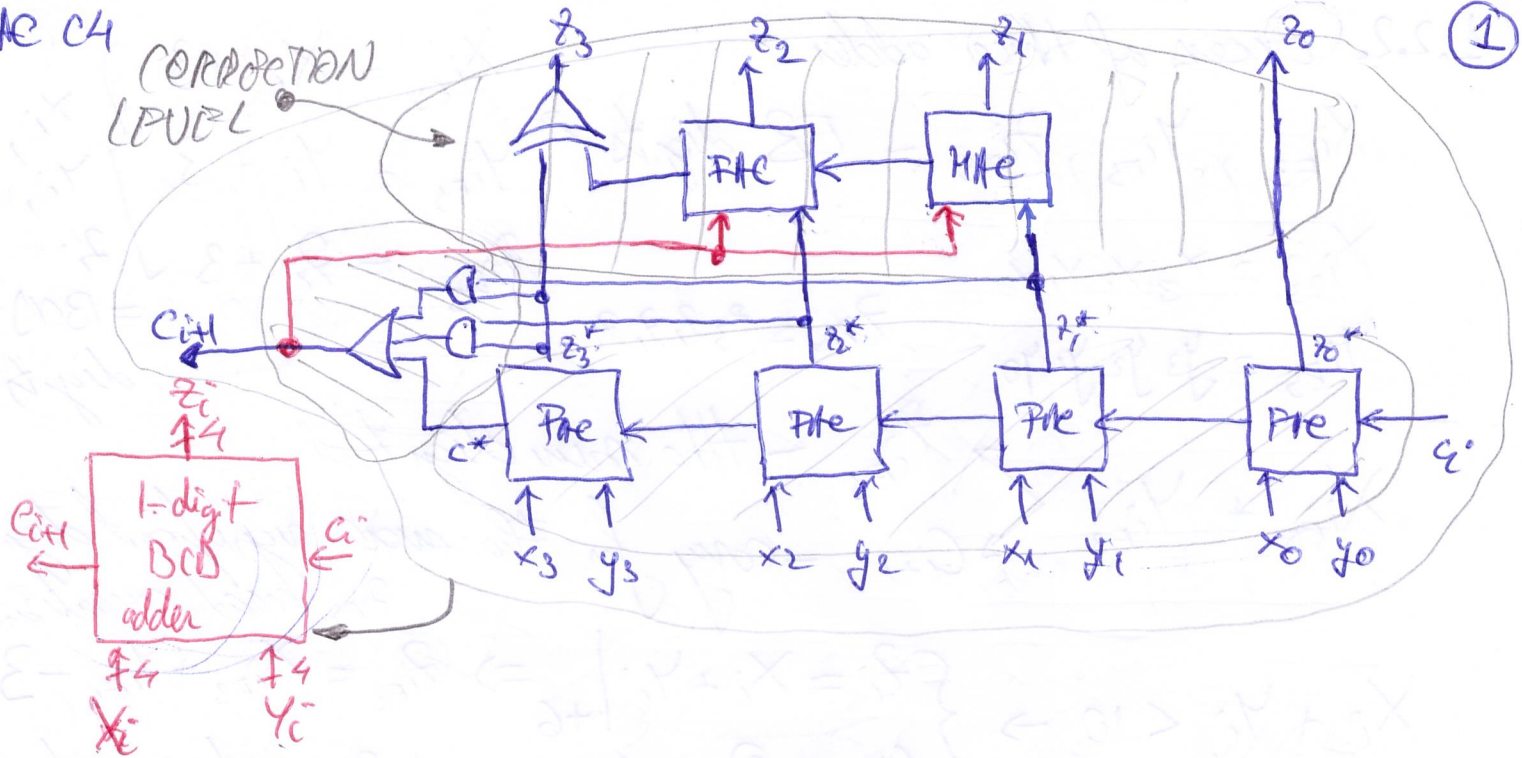



MC 04

CORRECTION  
LEVEL

①



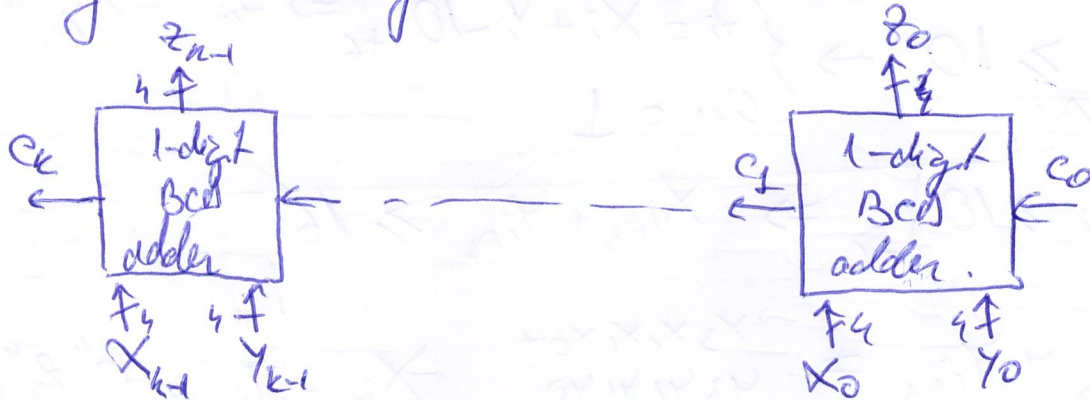Addition of 2  $k$ -digit BCD numbers:  $k$  cells:



Example:

$$\begin{array}{r} 683 + \\ 197 \\ \hline 880 \end{array}$$

$\begin{array}{r} 0110 + \\ 0001 \\ \hline 1000 \end{array}$ <p>8</p>	$\begin{array}{r} 1000 + \\ 1001 \\ \hline 10010 \end{array}$ <p>8</p>	$\begin{array}{r} 0011 + \\ 0111 \\ \hline 1010 \end{array}$ <p>0</p>
-----------------------------------------------------------------------	------------------------------------------------------------------------	-----------------------------------------------------------------------

Arrows indicate the carry propagation from the least significant digit to the most significant digit.

1.2.2. Excess of three adder.

$X_{iE3}, Y_{iE3}, z_{iE3}$  - EB digits  $\rightarrow$

$$X_{iE3} = x_3 x_2 x_1 x_0$$

$$Y_{iE3} = y_3 y_2 y_1 y_0$$

$$z_{iE3} = z_3 z_2 z_1 z_0$$

$$\left. \begin{aligned} X_{iE3} &= X_i + 3 \\ Y_{iE3} &= Y_i + 3 \\ z_{iE3} &= z_i + 3 \end{aligned} \right\} \begin{aligned} X_i, \\ Y_i, \\ z_i \end{aligned} = \text{BCD digits.}$$

$X_{iE3} + Y_{iE3} \rightarrow \begin{cases} z_{iE3} - \text{the sum digit} \\ C_{i+1} - \text{carry for the more significant digit} \end{cases}$

$$X_i + Y_i < 10 \rightarrow \begin{cases} z_i = X_i + Y_i \\ C_{i+1} = 0 \end{cases} \Rightarrow z_{iE3} = X_{iE3} + Y_{iE3} - 3$$

$z_i$  need correction

$$X_i + Y_i \geq 10 \rightarrow \begin{cases} z_i = X_i + Y_i - 10 \\ C_{i+1} = 1 \end{cases} \Rightarrow z_{iE3} = X_{iE3} + Y_{iE3} - 13$$

$z_i$  need correction

$$X_i + Y_i \geq 10 \mid_{+6} \Rightarrow X_{iE3} + Y_{iE3} \geq 16$$

$$X_{iE3} + Y_{iE3} = \begin{array}{cccc} x_3 & x_2 & x_1 & x_0 \\ y_3 & y_2 & y_1 & y_0 \\ \hline \end{array} \quad \text{(binary adder)} \quad C^4 \quad z_3^4 \quad z_2^4 \quad z_1^4 \quad z_0^4$$

$$X_{iE3} + Y_{iE3} = C^4 \quad z_3^4 \quad z_2^4 \quad z_1^4 \quad z_0^4$$

$$X_{iE3} + Y_{iE3} \geq 16 \equiv C^4 = 1$$

Subtracting 3 on 4 bits  $\equiv$  adding 13 on 4 bits.

$$(a + b - 3) \bmod 16 = (a + b - 3 + 16) \bmod 16 = (a + b + 13) \bmod 16$$

Subtracting 13 on 4 bits  $\equiv$  adding 3 on 4 bits.

$z_{iE3}$ 's correction depend:

$$\begin{aligned} & \begin{array}{c} 1 \\ \uparrow \\ C^4 \end{array} \xrightarrow{x_i + y_i \geq 10} \Rightarrow \begin{cases} z_{iE3} = z_3^4 \quad z_2^4 \quad z_1^4 \quad z_0^4 + \\ \quad \quad \quad 0 \quad 0 \quad 1 \quad 1 \\ C_{i+1} = 1 \end{cases} \end{aligned}$$

$$\begin{aligned} & \xrightarrow{x_i + y_i < 10} 0 \Rightarrow \begin{cases} z_{iE3} = z_3^4 \quad z_2^4 \quad z_1^4 \quad z_0^4 + \\ \quad \quad \quad 1 \quad 1 \quad 0 \quad 1 \\ C_{i+1} = 0 \end{cases} \end{aligned}$$




Correction stage

②

$$Z_{i+3} = \frac{z_3^4}{c^4} \frac{z_2^4}{c^4} \frac{z_1^4}{c^4} \frac{z_0^4}{c^4} +$$

CORRECTION LEVIES

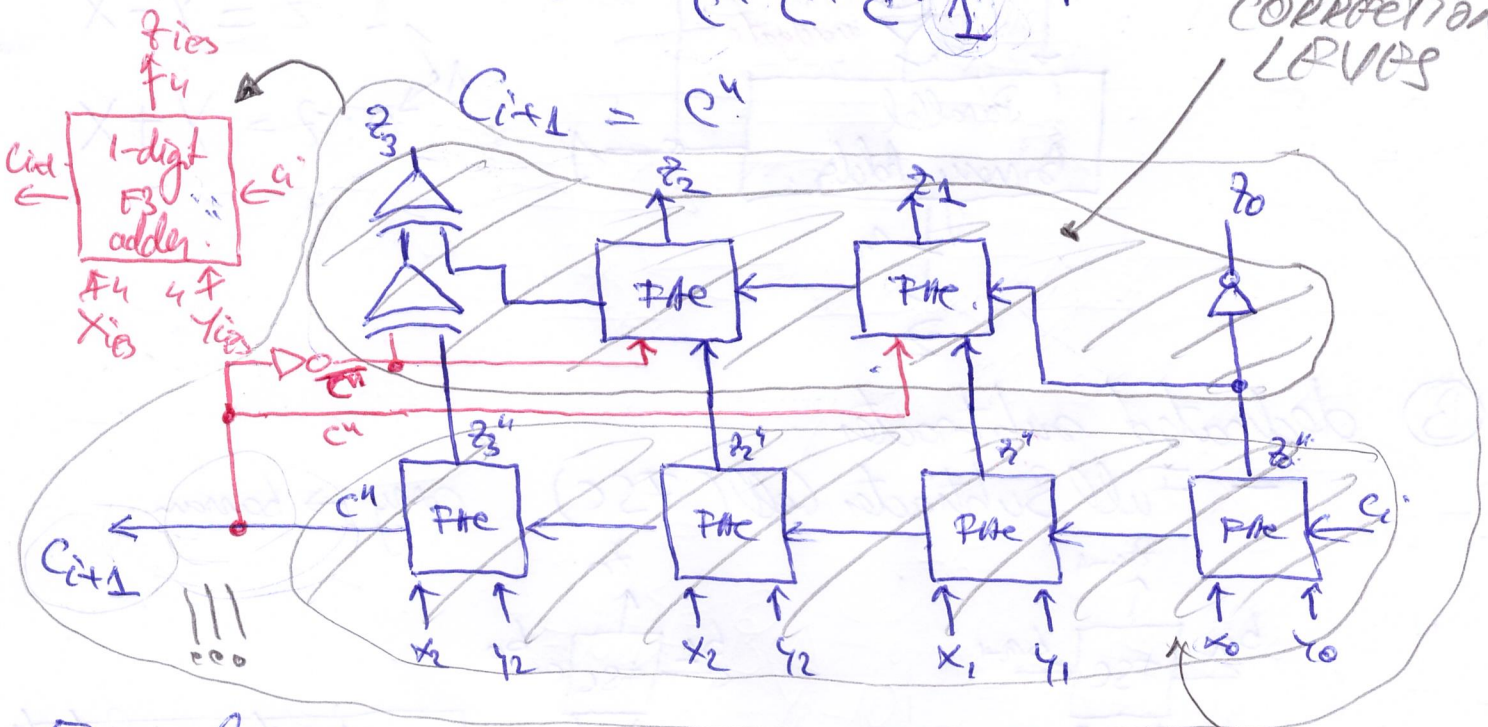

Example:

$$\begin{array}{r} 683 \\ 197 \\ \hline 880 \end{array}$$

$$\begin{array}{r} 1001 \\ 0100 \\ \hline 01110 \\ \rightarrow 1101 \\ * 1011 \\ \hline 8 \end{array} \quad \begin{array}{r} 1011 \\ 1100 \\ \hline 11000 \\ \rightarrow 0011 \\ 1011 \\ \hline 8 \end{array} \quad \begin{array}{r} 0110 \\ 1010 \\ \hline 10000 \\ \rightarrow 0011 \\ 0011 \\ \hline 0 \end{array} +$$

BINARY ADDER

Advantages: -  $C_{i+1}$  faster generation  
 $\rightarrow$  faster addition  
 - can use binary adders  
 $\rightarrow$  has access to interrelated carries

1.3. Subtractors based on Serial Propagation of Carry / Borrow

$X$  = subtrahend


$Y$  = subtractor

$$Z = Y - X$$

$$X = x_{n-1} x_{n-2} \dots x_1 x_0$$

$$Y = y_{n-1} y_{n-2} \dots y_1 y_0$$

① use binary adder.  $Y - X = Y + (-X)$


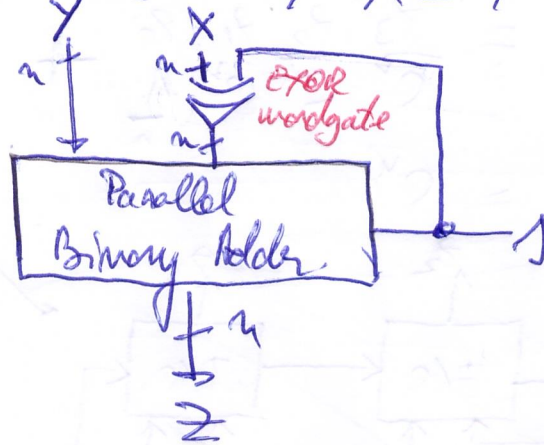


1:  $Z = Y - X$   
0:  $Z = Y + X$

② dedicated subtractor.

— Full Subtractor Cell (FSC)

carry  $\rightarrow$  borrow

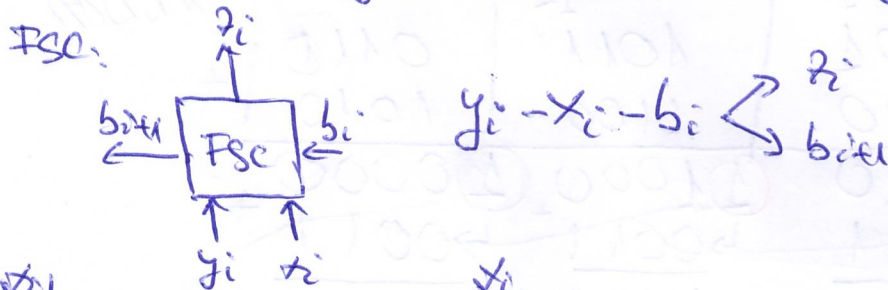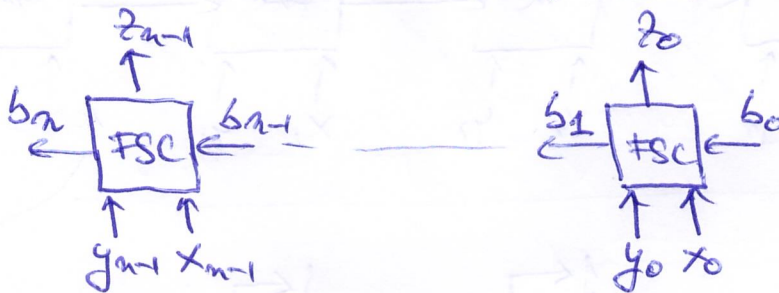

Inputs			Outputs	
$y_i$	$x_i$	$b_i$	$z_i$	$b_{i+1}$
0	0	0	0	0
1	0	0	1	0
0	1	0	1	1
1	1	0	0	1
1	0	1	1	0
1	0	1	0	0
1	1	0	0	0
0	1	1	1	1


$1 - 1 - 1 = 0 - 0 - 1$

$z_i = x_i \oplus y_i \oplus b_i$

$y_i$	$x_i$	$b_i$	$z_i$	$b_{i+1}$
0	0	0	0	0
1	0	0	1	0
0	1	0	1	1
1	1	0	0	1

$b_{i+1} = \bar{y}_i \bar{b}_i + \bar{y}_i x_i + b_i x_i$

$y_i$	$x_i$	$b_i$	$b_{i+1}$
0	0	0	0
1	0	0	0
0	1	0	1
1	1	0	1

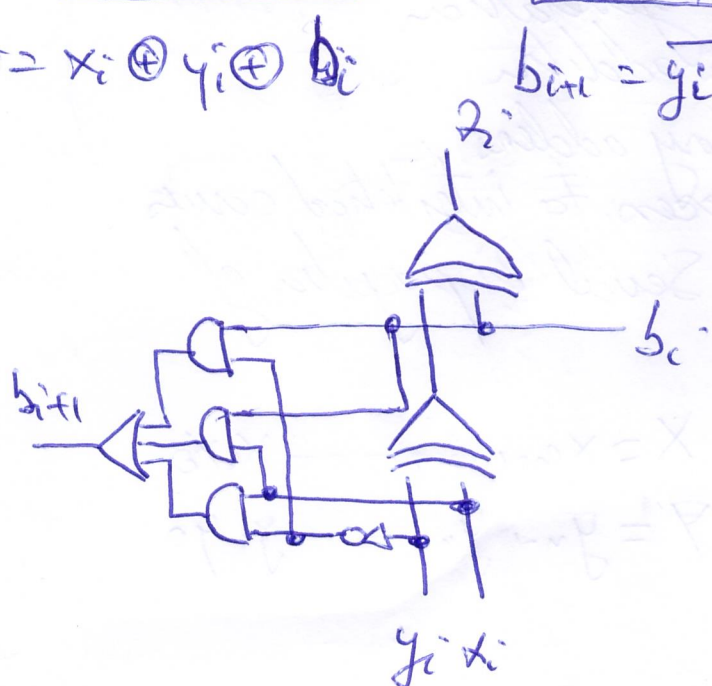



© BCD subtraction

(3)

Let  $X^{(k)}, Y^{(k)}$  - BCD numbers,  $k$ -digits

$$Z^{(k)} = Y^{(k)} - X^{(k)}$$

$$Y^{(k)} = Y_{k-1} Y_{k-2} \dots Y_0$$

$$X^{(k)} = X_{k-1} X_{k-2} \dots X_0$$

Let 9's complement of a BCD digit  $X_i$

$$X_i^* = 9 - X_i$$

$\Rightarrow$  9's complement of a BCD number on  $k$  digits,  $X^{(k)}$

$$\overline{X^{(k)}}^* = \overline{X_{k-1}}^* \overline{X_{k-2}}^* \dots \overline{X_0}^* =$$

$$\overline{X^{(k)}}^* = 10^k - 1 - X^{(k)}$$

$$Z^{(k)} = (Y^{(k)} - X^{(k)}) \bmod 10^k =$$

$$= (Y^{(k)} + \underbrace{10^k - 1 - X^{(k)}}_{\overline{X^{(k)}}^*} + 1) \bmod 10^k$$

$$= (Y^{(k)} + \overline{X^{(k)}}^* + \underline{1}) \bmod 10^k$$

9's Complementing of a BCD digit.

$$X_i = x_3 x_2 x_1 x_0 \rightarrow \overline{X_i^*} = x_3^* x_2^* x_1^* x_0^*$$

$$\overline{X_i^*} = 9 - X_i$$

Inputs				Outputs			
$x_3$	$x_2$	$x_1$	$x_0$	$x_3^*$	$x_2^*$	$x_1^*$	$x_0^*$
0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	1
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0


! don't care.  $x_3 x_2 x_1 x_0 \in [10; 15]$

$$X_3^* = \overline{X_3 + X_2 + X_1}$$


$$X_2^* = X_2 \oplus X_1$$

$$X_1^* = X_1$$

$$X_0^* = \overline{X_0}$$

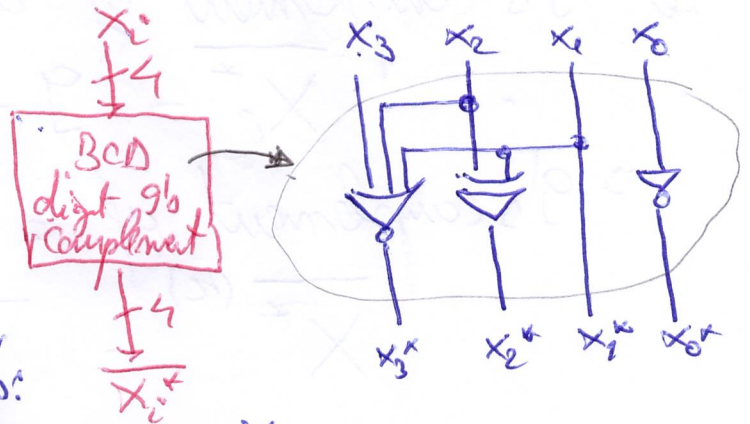

Subtracting 2 BCD nos., on k digits:

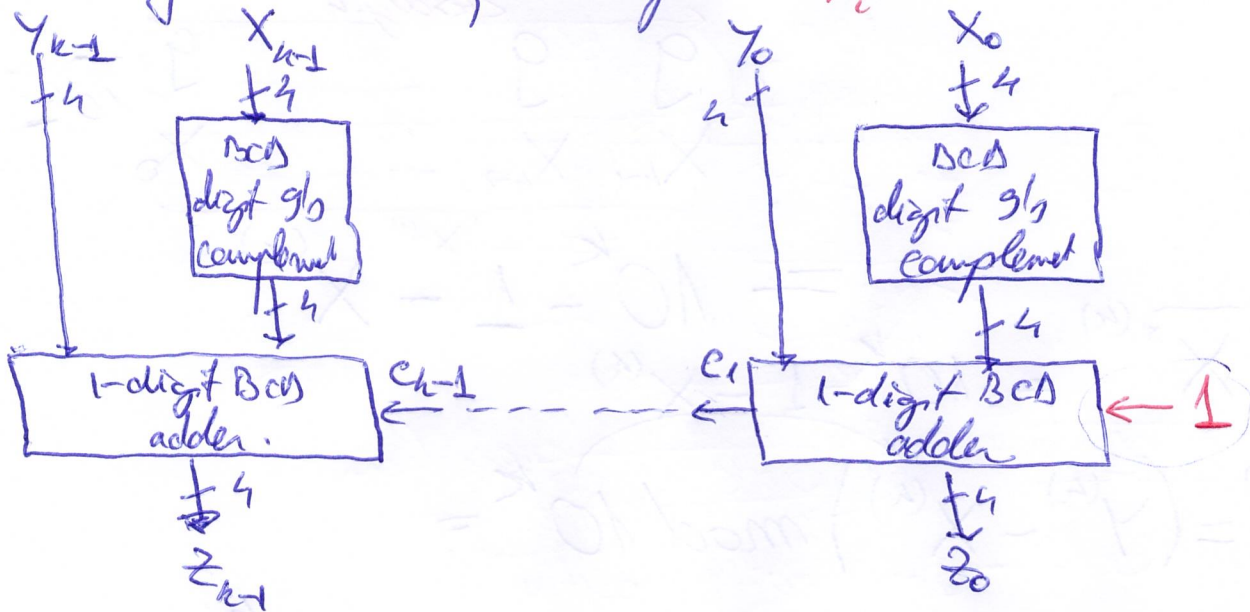

1.4. Parallel Computation of Sum