

Ac c3

Addition's special cases

- carry out from msb
- zero result
- negative result
- overflow

①

Overflow: result exceeds capacity

a) for unsigned: X, Y, integers, 3 bit on 4 bit

$$X = 5$$

$$Y = 6$$

$$\begin{array}{r} 101 \\ + 110 \\ \hline \end{array}$$

$$\text{✗ } 011 = \text{✗}$$

← 3 →
storing capacity

$$\begin{array}{r} 0101 \\ + 0110 \\ \hline 1011 \end{array}$$

11 = 1011 ✓
← 4 →
storing capacity

for unsigned, overflow \equiv carry out from msb

b) for signed: X, Y integers, in C2, 4 bit on 5 bit

$$X = +5$$

$$Y = +6$$

$$\begin{array}{r} 0101_{C2} \\ + 0110_{C2} \\ \hline 1011_{C2} = \text{✗} \end{array}$$

sign ↓ ↓ ↓
 $1101_{S1} = -5$

$$\begin{array}{r} 00101_{C2} \\ + 00110_{C2} \\ \hline 01011_{C2} \\ = +11 \end{array}$$

$$\begin{array}{r} -5 = 1011_{C2} \\ -6 = 1010_{C2} \\ \hline \text{✗ } 0101_{C2} = \text{✗} \end{array}$$

for signed, overflow \equiv adding same sign operand
the result has opposite sign

Q:

$$\begin{array}{r} 1111 = -1 \\ 0111 = +7 \\ \hline \text{✗ } 0110 = +6 \end{array}$$

sign X \neq sign Y. sign X = +; sign Y = -
 $X + Y \equiv$ subtraction.

$$|X| - |Y| = Z \leq \max\{|X|, |Y|\}$$

Overflow for signed.

X, Y - n bits, in C2, integers

$$X_{C2} + Y_{C2} = Z_{C2}$$

overflow $\stackrel{\text{def}}{=} \vee$

$$\begin{array}{r} X_{n-1} \text{ sign of } X \\ Y_{n-1} \text{ } Y \\ Z_{n-1} \text{ } Z \end{array}$$

Inputs			Outputs	
x_{n-1}	y_{n-1}	C_{n-1}	z_{n-1}	V
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

Boolean identities:

$$I_1: (A \oplus B) \cdot C = A \cdot C \oplus B \cdot C$$

$$I_2: A + B = A \oplus B \oplus A \cdot B$$

$$I_2': A \oplus B = (A + B) \oplus A \cdot B$$

$$X \oplus 0 = X$$

$$\overline{C_{n-1}} = 1 \oplus C_{n-1}$$

$$V = \overline{x_{n-1}} \overline{y_{n-1}} C_{n-1} + x_{n-1} y_{n-1} \overline{C_{n-1}} = I_2$$

$$\overline{x_{n-1}} \overline{y_{n-1}} C_{n-1} \oplus x_{n-1} y_{n-1} \overline{C_{n-1}} \oplus (\overline{x_{n-1}} \overline{y_{n-1}} C_{n-1} \oplus x_{n-1} y_{n-1} \overline{C_{n-1}})$$

$$= \overline{x_{n-1}} \overline{y_{n-1}} C_{n-1} \oplus x_{n-1} y_{n-1} (1 \oplus C_{n-1}) = I_1$$

$$\overline{x_{n-1}} \overline{y_{n-1}} C_{n-1} \oplus x_{n-1} y_{n-1} C_{n-1} \oplus x_{n-1} y_{n-1} = I_1$$

$$(\overline{x_{n-1}} \overline{y_{n-1}} \oplus x_{n-1} y_{n-1}) C_{n-1} \oplus x_{n-1} y_{n-1} = I_2'$$

$$(\overline{x_{n-1}} \overline{y_{n-1}} + x_{n-1} y_{n-1}) C_{n-1} \oplus x_{n-1} y_{n-1} =$$

$$\overline{x_{n-1} \oplus y_{n-1}} = x_{n-1} \oplus y_{n-1} \oplus 1$$


$$(x_{n-1} \oplus y_{n-1} \oplus 1) C_{n-1} \oplus x_{n-1} y_{n-1} = I_2'$$

$$x_{n-1} C_{n-1} \oplus y_{n-1} C_{n-1} \oplus x_{n-1} y_{n-1} \oplus C_{n-1} =$$

$$(x_{n-1} C_{n-1} + y_{n-1} C_{n-1} + x_{n-1} y_{n-1}) \oplus C_{n-1} = C_n$$

$$V = C_n \oplus C_{n-1}$$

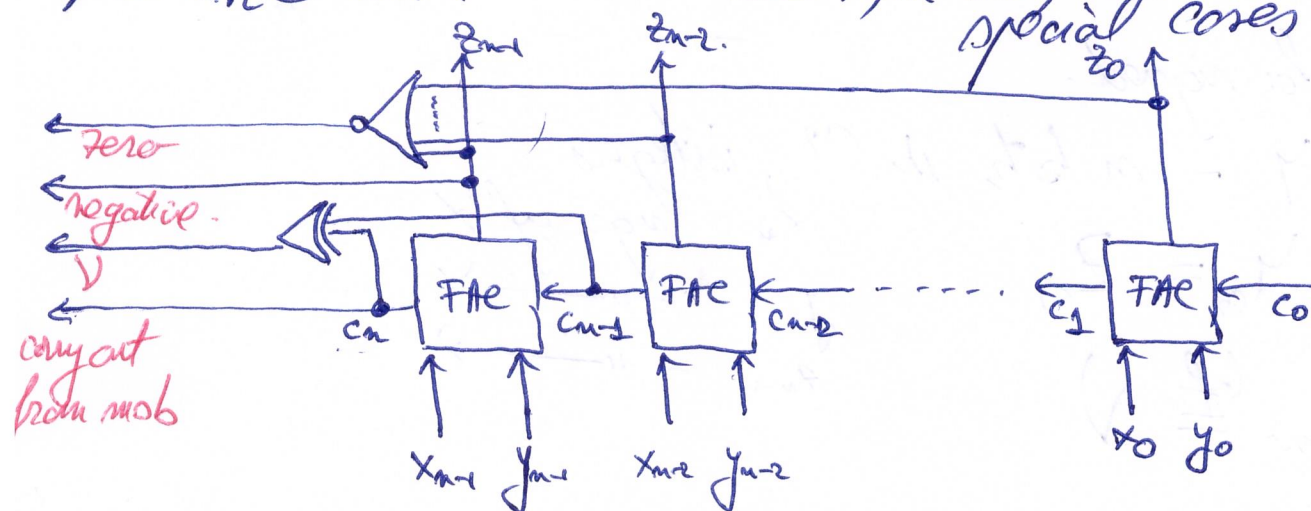RCA, n bits, with additional special cores



Addition with constant - only odd constants

(2)


$$Y = \text{constant} \quad Y = y_{m-1} y_{m-2} \dots y_0$$

$$X = x_{m-1} x_{m-2} \dots x_0$$

$$Z = z_{m-1} z_{m-2} \dots z_0$$

$$Z = X + Y$$
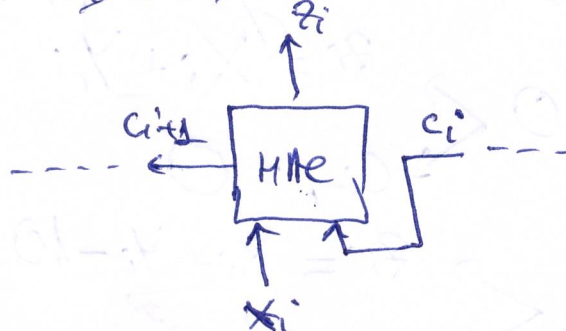
$$\text{if } y_i = 0 \quad \left\{ \begin{aligned} z_i &= x_i \oplus 0 \oplus c_i = x_i \oplus c_i \\ c_{i+1} &= x_i \cdot 0 + 0 \cdot c_i + x_i \cdot c_i = x_i \cdot c_i \end{aligned} \right\} \text{HAC}$$





$$\text{if } y_i = 1$$

$$z_i = x_i \oplus 1 \oplus c_i = \overline{x_i} \oplus c_i$$

$$c_{i+1} = x_i \cdot 1 + 1 \cdot c_i + x_i \cdot c_i = x_i + c_i + x_i \cdot c_i$$

$$= x_i(1 + c_i) + c_i = x_i + c_i$$
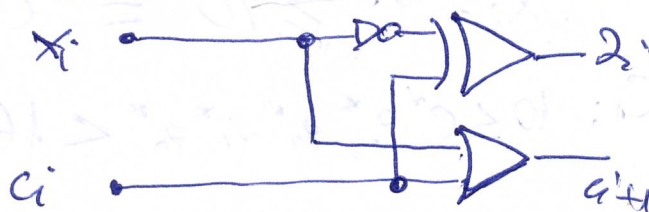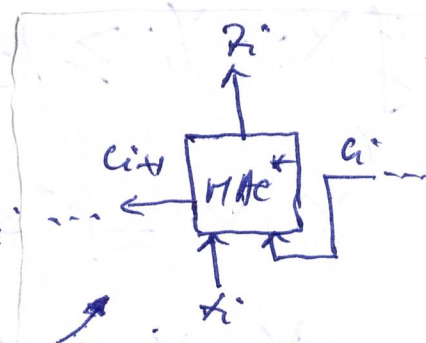
$$\left\{ \begin{aligned} z_i &= \overline{x_i} \oplus c_i \\ c_{i+1} &= x_i + c_i \end{aligned} \right\} \text{HAC}^*$$



Example: X, Y 6-bit

$$Y = y_5 y_4 y_3 y_2 y_1 y_0 \quad X = x_5 x_4 x_3 x_2 x_1 x_0 \quad Z = X + Y$$

$$= \underline{110100}$$

$$\begin{array}{r} x_3 \quad x_1 \quad x_0 \\ 1 \quad 0 \quad 0 \end{array}$$

$$z_2 = x_2 + y_2, c_2 = 0$$

$$z_2 = x_2 \oplus y_2 \oplus c_2 =$$


$$= \underline{x_2} \oplus 1 \oplus 0 =$$

$$z_2 = \underline{x_2}$$

$$c_3 = x_2 \cdot y_2 + x_2 \cdot c_2 + y_2 \cdot c_2$$

$$= x_2 \cdot 1 + x_2 \cdot 0 + 1 \cdot 0$$

$$c_3 = x_2$$

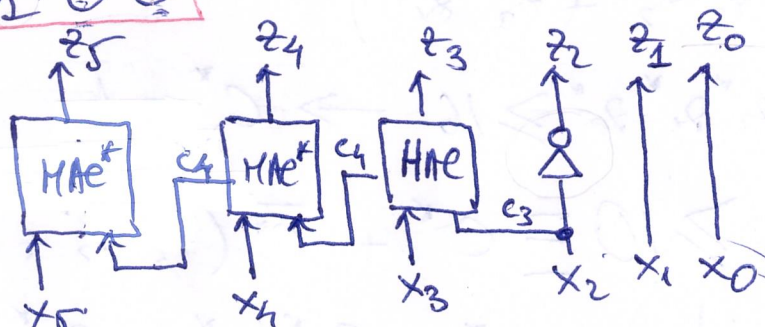

1.2. Decimal Adders based on Serial Carry Propagation

1.2.1. BCD adder.

BCD

53

Let X_i, Y_i, Z_i - BCD 8421 digits.

$$X_i = x_3 x_2 x_1 x_0 \quad Y_i = y_3 y_2 y_1 y_0 \quad Z_i = z_3 z_2 z_1 z_0$$

$$X_i + Y_i \begin{cases} Z_i = \text{sum digit} \\ C_{i+1} = \text{carry out for next digit} \end{cases}$$

$$\text{if } X_i + Y_i < 10 \begin{cases} Z_i = X_i + Y_i \\ C_{i+1} = 0 \end{cases}$$

$$5 - 0101$$

$$3 - \frac{0011}{1000} = 8$$

$$7 - 0111$$

$$8 - \frac{1000}{1111} = 15$$

$$\text{CORRECTION } (15)_{10}$$

$$\text{if } X_i + Y_i \geq 10 \begin{cases} Z_i = X_i + Y_i - 10 \\ C_{i+1} = 1 \end{cases}$$

$$X_i + Y_i = C^* z_3^* z_2^* z_1^* z_0^*$$

$$X_i + Y_i \geq 10 \equiv C^* z_3^* z_2^* z_1^* z_0^* \geq 10$$

$$\begin{cases} 10 \leq C^* z_3^* z_2^* z_1^* z_0^* < 16 \\ C^* z_3^* z_2^* z_1^* z_0^* \geq 16 \end{cases}$$

$$C_1: 10 \leq C^* z_3^* z_2^* z_1^* z_0^* < 16$$

$$C^* = 0 (\leq 16)$$

$$z_3^* z_2^* z_1^* z_0^* \geq 10$$

$$z_3^* z_2^* z_1^* z_0^* \geq 10 \text{ then } z_3^* z_2^* + z_3^* z_1^* = 1$$

$$C_1: \overline{C^*} (z_3^* z_2^* + z_3^* z_1^*)$$

$$C_2: C^* z_3^* z_2^* z_1^* z_0^* \geq 16 \rightarrow C^* = 1$$

$$X_i + Y_i \geq 10 \equiv C^* + \overline{C^*} (z_3^* z_2^* + z_3^* z_1^*)$$

$$a + (\overline{a})b = a + b$$

$$\rightarrow C^* + z_3^* z_2^* + z_3^* z_1^*$$

How to subtract $10_{(10)}$ from $X_i + Y_i$

$$(a+b) \bmod c = (a+b+c) \bmod c$$

$$(X_i + Y_i - 10) \bmod 2^4 = (X_i + Y_i - 10) \bmod 16$$

$$= (X_i + Y_i + 16 - 10) \bmod 16 = (X_i + Y_i + 6) \bmod 16$$

$z_3^* z_2^*$	00	01	11	10
00				
01				
11	1	1	1	1
10			1	1

subtracting 10 from $X_i + Y_i \equiv$ adding 6 to $X_i + Y_i$ (3)

Ex:
$$\begin{array}{r} 15 - \\ 10 \\ \hline 5 \end{array} = \begin{array}{r} 1111 \\ 1010 \\ \hline 0101 \end{array}$$

$$\begin{array}{r} 18 - \\ 10 \\ \hline 8 \end{array} = \begin{array}{r} 10010 \\ 1010 \\ \hline 1000 \end{array}$$

$$\begin{array}{r} 15 + \\ 6 \\ \hline \end{array} = \begin{array}{r} 1111 \\ 0110 \\ \hline \end{array}$$

$$\begin{array}{r} 18 + \\ 6 \\ \hline \end{array} = \begin{array}{r} \cancel{1}0010 \\ 0110 \\ \hline 1000 \end{array}$$

z_i 's correction depends on:

$$c^* + z_3^* z_2^* + z_3^* z_1^* \begin{cases} \xrightarrow{1} (X_i + Y_i \geq 10) \Rightarrow \begin{cases} z_i = z_3^* z_2^* z_1^* z_0^* + 0110 (+6) \\ c_{i+1} = 1 \end{cases} \\ \xrightarrow{0} (X_i + Y_i < 10) \Rightarrow \begin{cases} z_i = z_3^* z_2^* z_1^* z_0^* + 0000 (0) \\ c_{i+1} = 0 \end{cases} \end{cases}$$

Correction stage for z_i

$$z_i = z_3^* z_2^* z_1^* z_0^* + 0c_{i+1}c_{i+1}0$$

and $c_{i+1} = c^* + z_3^* z_2^* + z_3^* z_1^*$